

Experiment 4 – Integrated System

Ali Keramati

810198519

I. FREQUENCY MULTIPLIER

Figure 1 shows state diagram of the controller.

And Figure 2 shows waveform testbench.

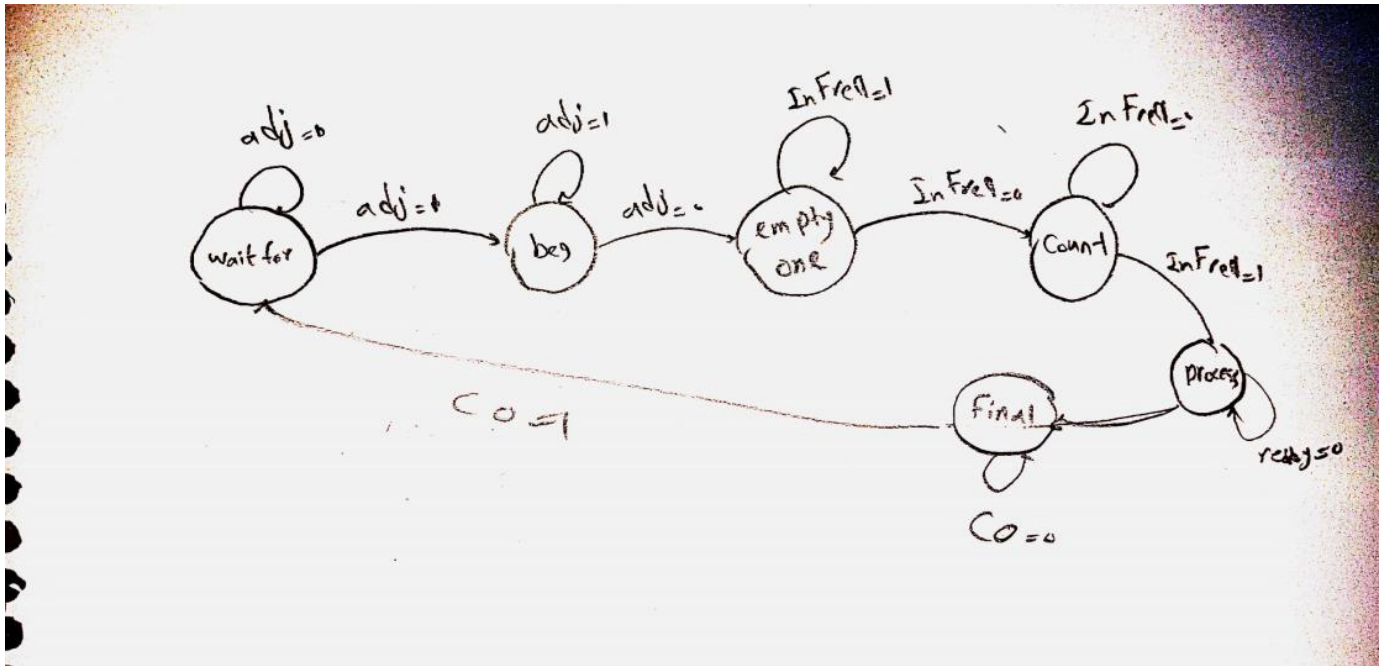


Figure 1

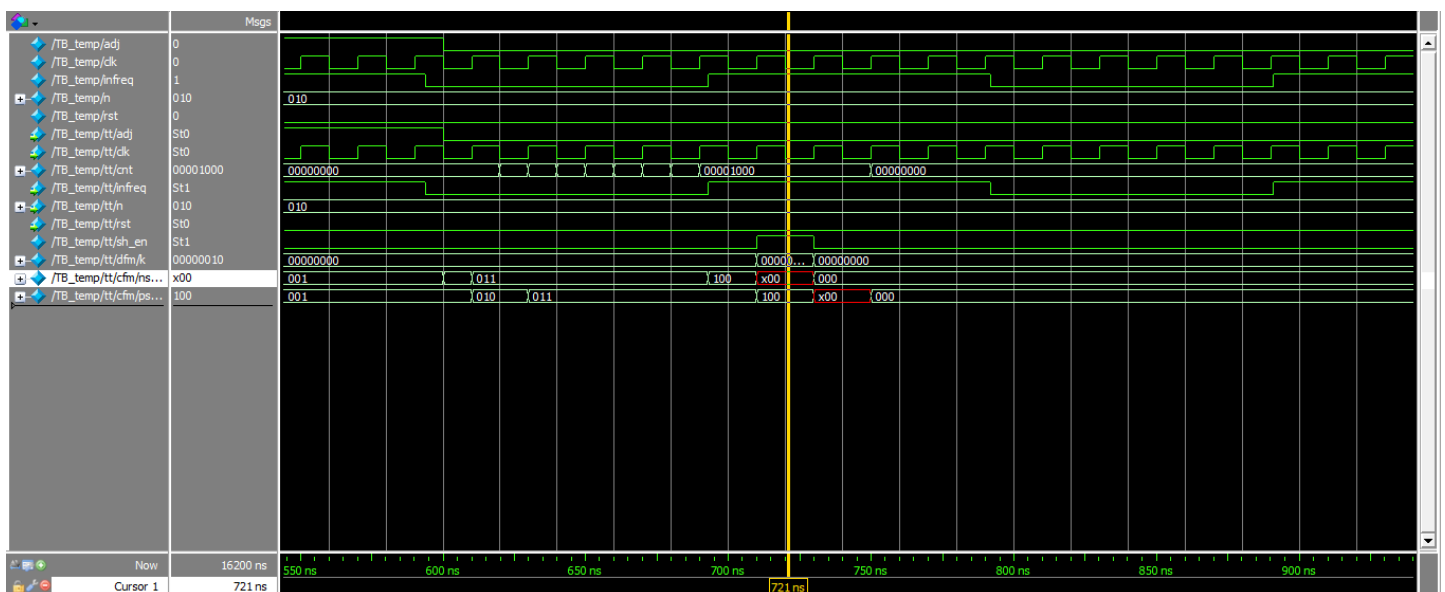


Figure 2

A. Exponential Engine

II. EXPONENTIAL ACCELERATOR

In Figure 3 we can see three outputs for different values for x.

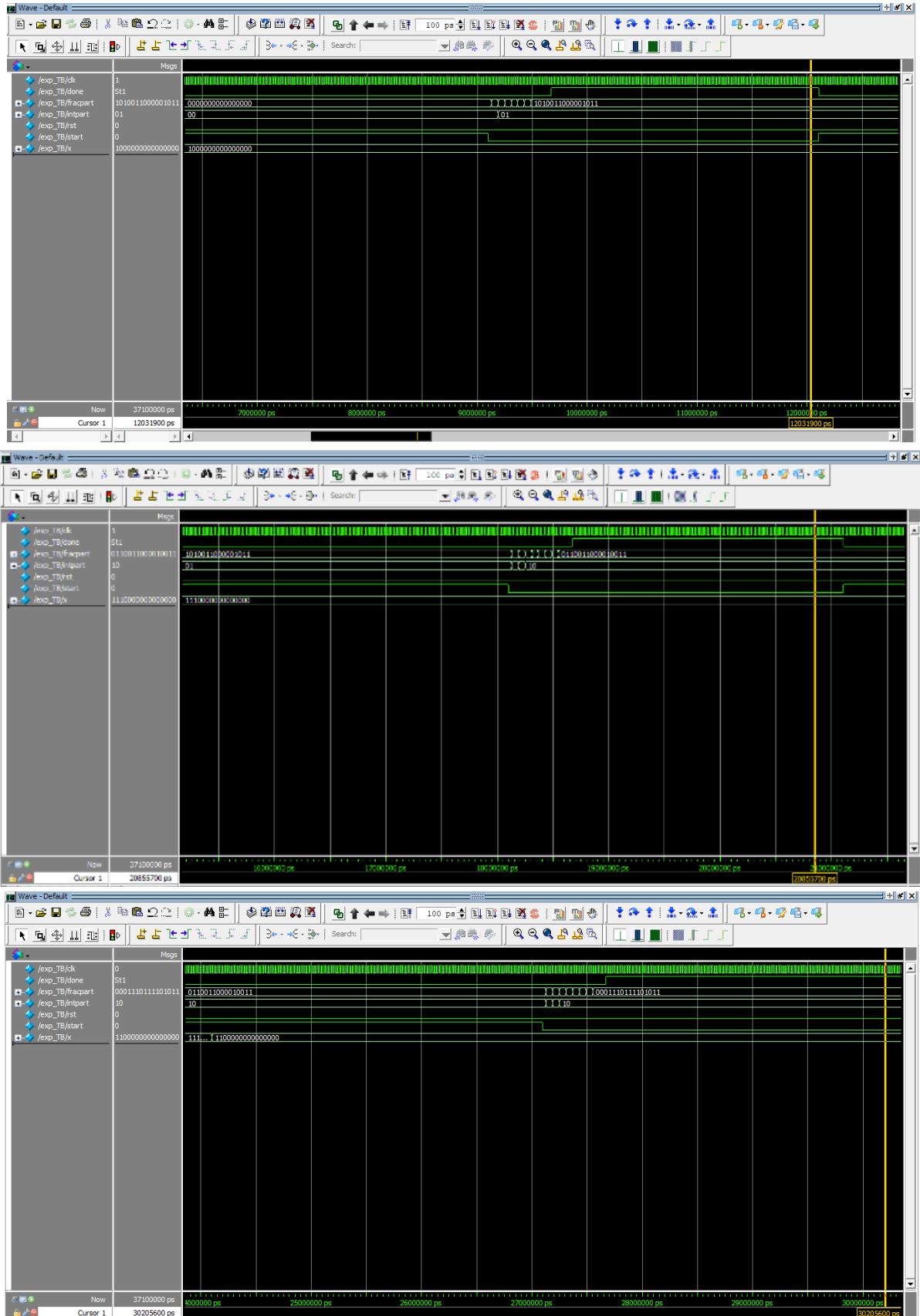


Figure 3

And in figure 4 we can see synthesis report. And Figure 5 shows timing analysis.

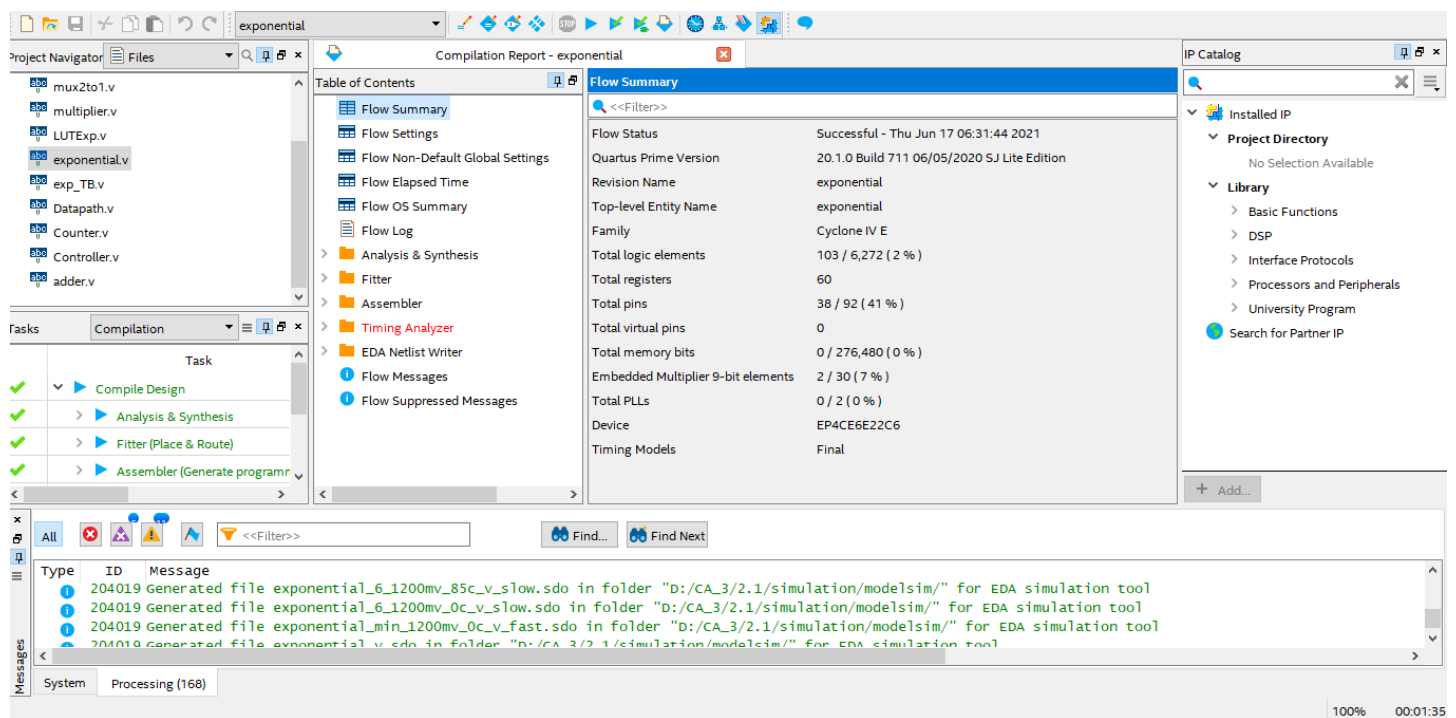


Figure 4

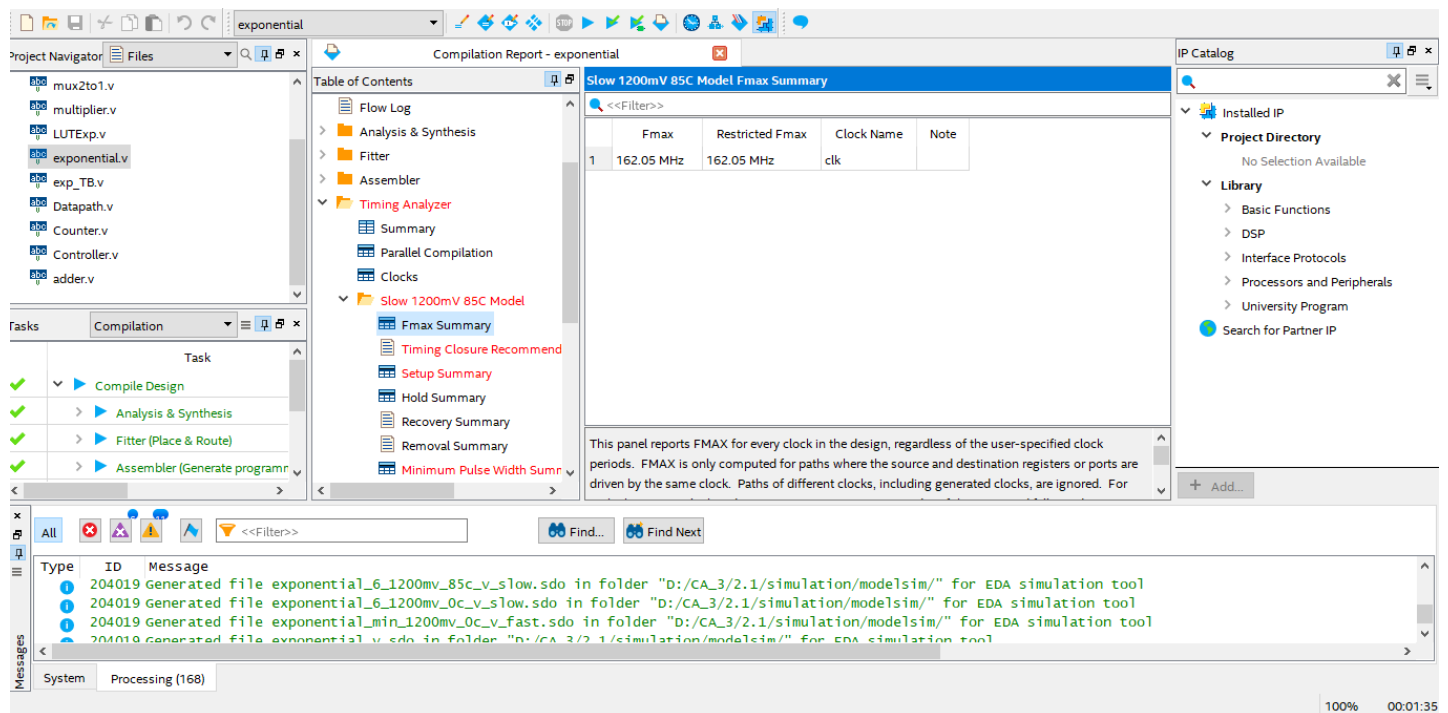


Figure 5

B. Exponential Accelerator wrapper

Figure 6 shows state diagram of controller of this part. And Figure 7 shows sunthesised model.
And Figure 8 shows output wave form.

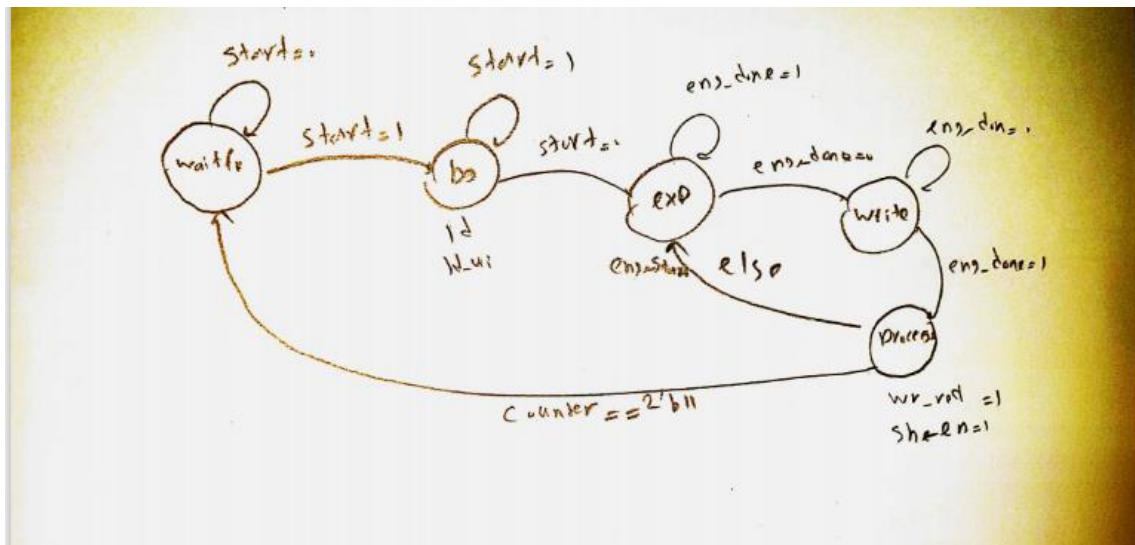


Figure 6

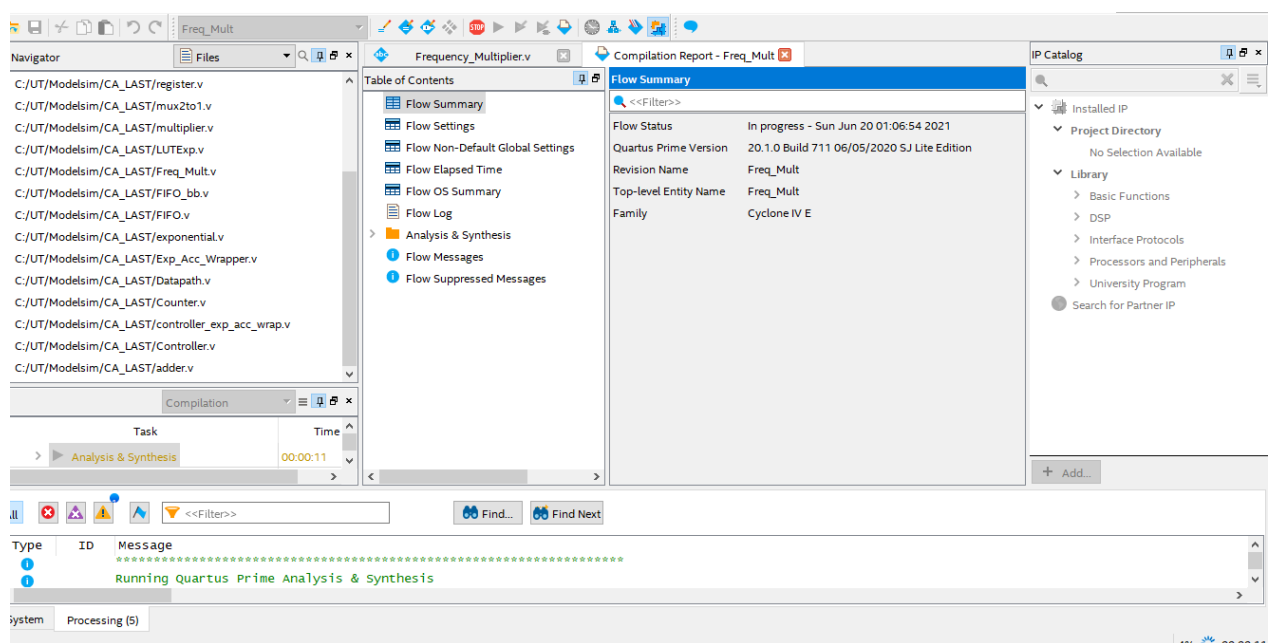


Figure 7

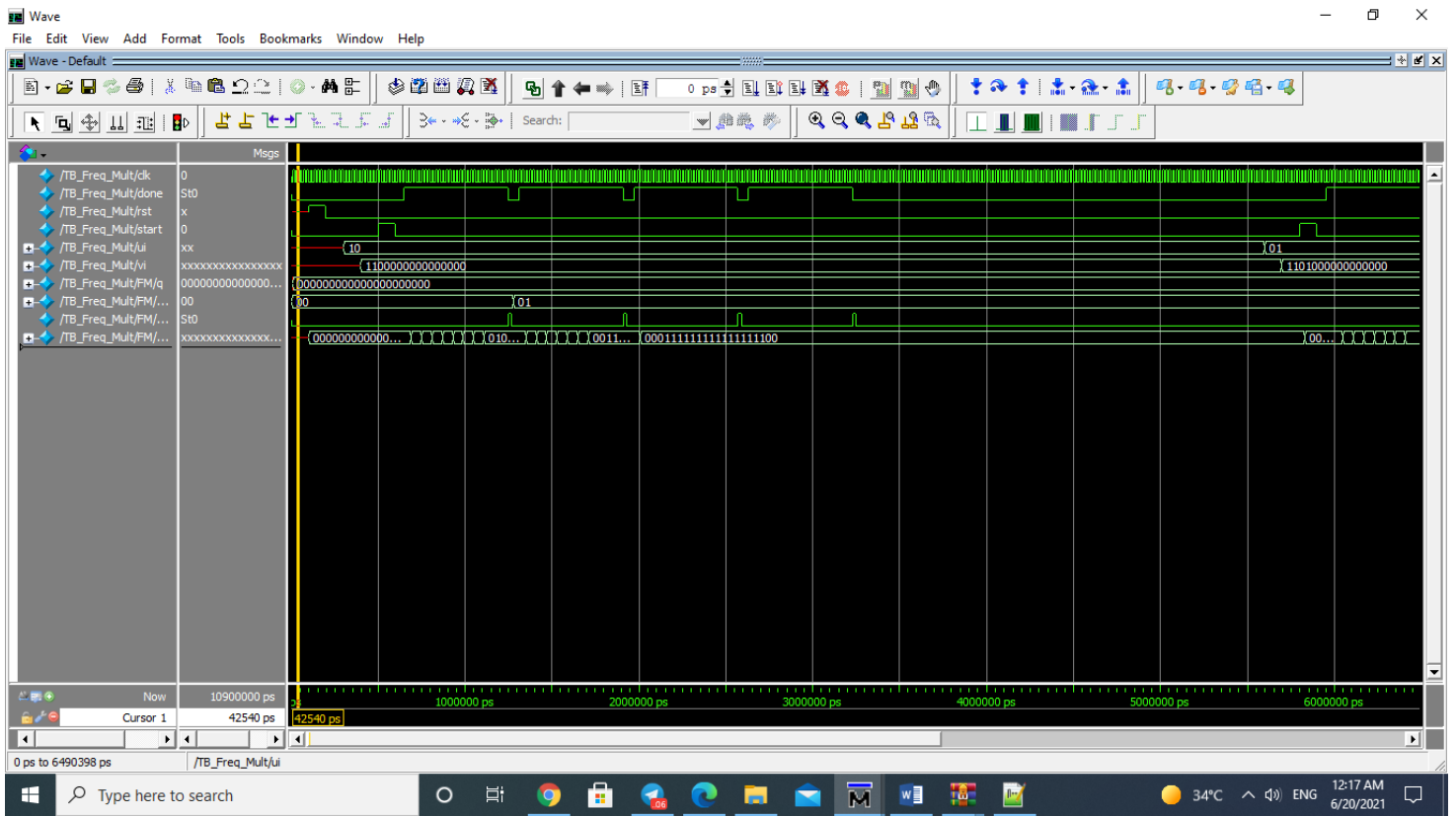


Figure 8

FOR PART 3 I didn't synthesis I
just write testbench and top level.